

DIGITAL LOGIC

Chapter 4 : Arithmetic Circuit


2024 Fall

This PowerPoint is for internal use only at Southern University of Science and Technology.
Please do not repost it on other platforms without permission from the instructor.

Today's Agenda

- Recap
- Context
 - Binary Adder-Subtractor
 - Decimal Adder
 - Binary Multiplier
- Reading: Textbook, Chapter 4.5-4.7

Recap

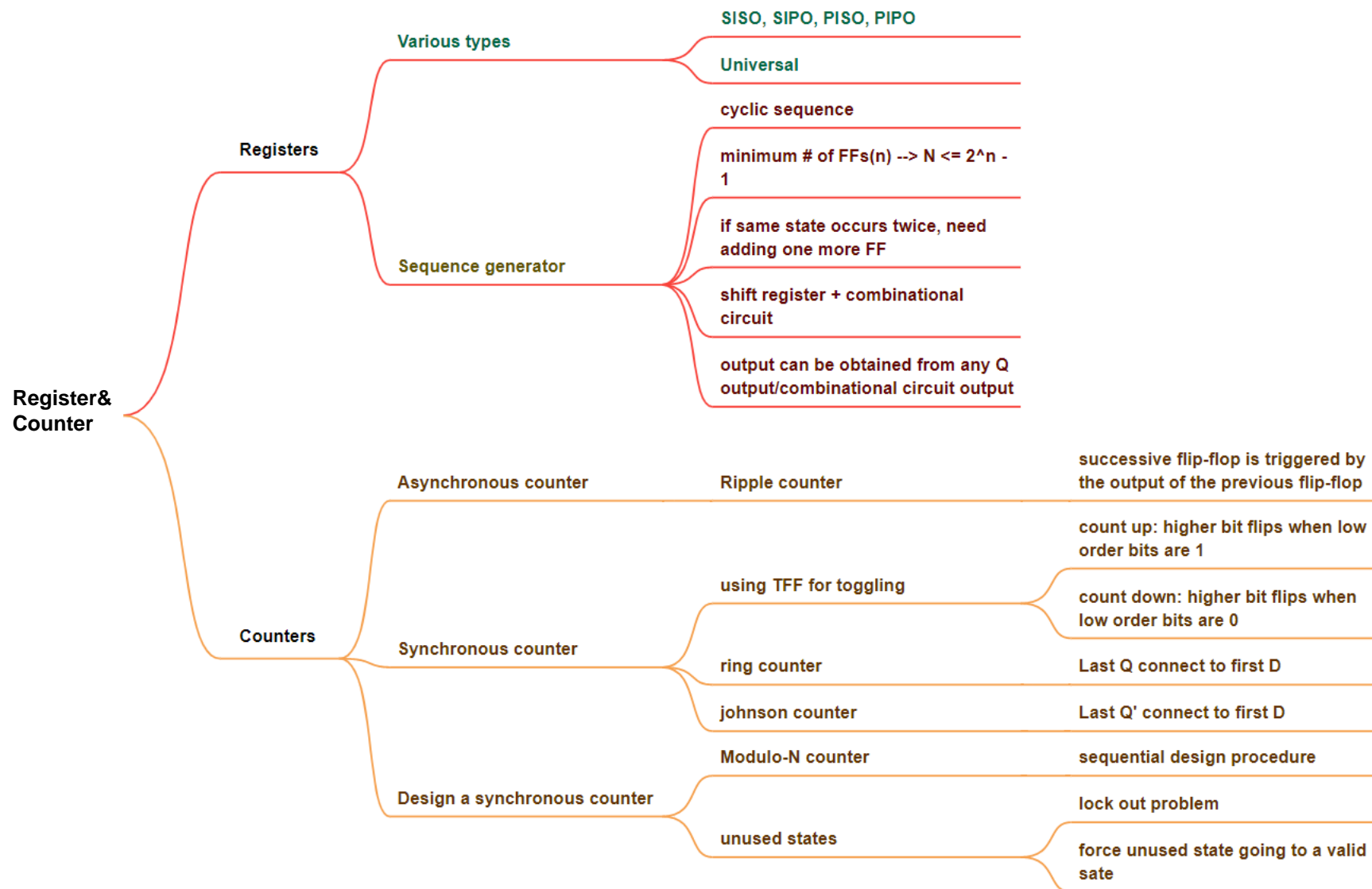

Outline

- **Binary Adder**
- Binary Subtractor
- Decimal Adder (BCD)
- Binary Multiplier
- Other Arithmetic Functions

Binary Add

- Similar to the addition operation of decimal numbers.
- $0+0 = 0$, $0+1 = 1$, $1+0 = 1$, $1+1 = 10$ ← The higher significant bit is called a **carry** (进位).
- A combinational circuit that performs the addition of two bits as described above is called a **half-adder**.
- The addition operation involves three bits — the **augend bit**, **addend bit**, and the **carry bit** and produces a sum result as well as carry.
- The combinational circuit performing this type of addition operation is called a **full-adder**.

| | |
|-------|-------------|
| 11 | carry(进位) |
| 1011 | augend(被加数) |
| 0001 | addend(加数) |
| <hr/> | |
| 1100 | sum |

Recall: Design Procedure

1. Specification: From the specifications, determine the inputs, outputs, and their symbols.
2. Formulation: Derive the truth table (functions) from the relationship between the inputs and outputs
3. Optimization: Derive the simplified Boolean functions for each output function. Draw a logic diagram for the resulting circuits using AND, OR, and inverters.
4. Technology Mapping: Transform the logic diagram to a new diagram using the available implementation technology.
 - Verification: Verify the design.

Half-adder

• 1. Spec

- Inputs: x , y
- Outputs: C (carry), S (sum)

• 2. Truth table


| | | 2^1 | 2^0 |
|-----|-----|-------|-------|
| x | y | C | S |
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

• 3. Boolean function


$$S = x'y + xy' = x \oplus y$$

$$C = xy$$

• 4. Block diagram

 

Full-adder

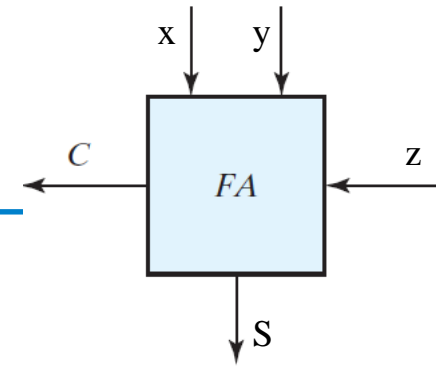

- 1. Spec
 - Inputs: x, y, z (carry from previous lower significant bit)
 - Outputs: C (carry), S (sum)

2. Truth table

3. Boolean function

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

| x | y | z | C | S |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

| | | | | |
|--------|------------------|------------------|------------------|------------------|
| x \ yz | y | | | |
| | 00 | 01 | 11 | 10 |
| 0 | m ₀ | m ₁ 1 | m ₃ | m ₂ 1 |
| 1 | m ₄ 1 | m ₅ | m ₇ 1 | m ₆ |

(a) $S = x'y'z + x'yz' + xy'z' + xyz$

xor gate, odd number
of 1 \rightarrow sum = 1

| | | | | |
|--------|----------------|------------------|------------------|------------------|
| x \ yz | y | | | |
| | 00 | 01 | 11 | 10 |
| 0 | m ₀ | m ₁ | m ₃ 1 | m ₂ |
| 1 | m ₄ | m ₅ 1 | m ₇ 1 | m ₆ 1 |

(b) $C = xy + xz + yz$

if \geq two inputs are 1
 \rightarrow carry = 1



Full-adder

- 3. Boolean function

$$S = x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z$$

$$C = xy + xz + yz$$

- 4. Block diagram

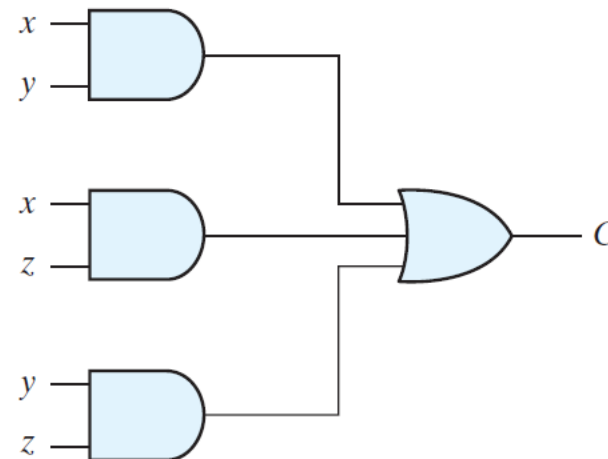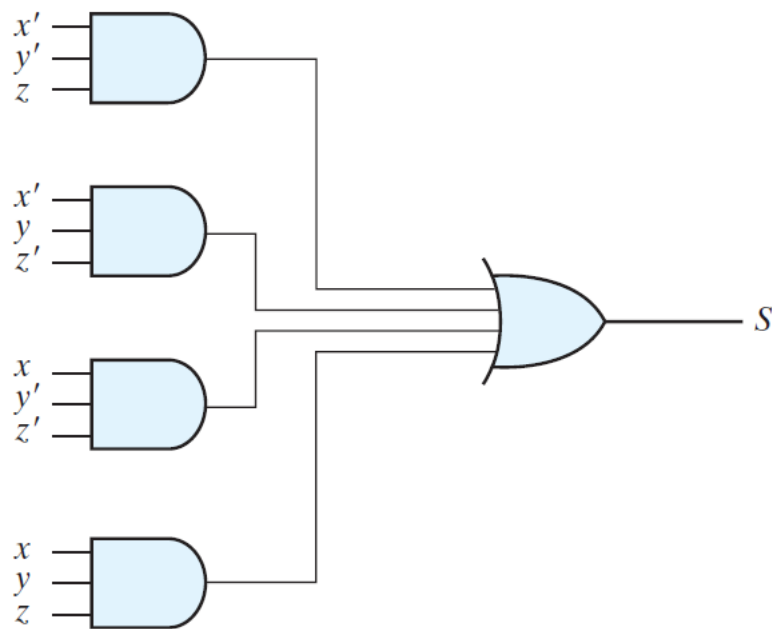


Full Adder Implemented with Half Adders

- Full adder implemented with: Two half adders and one OR gate

$$\begin{aligned} S &= xy'z' + x'yz' + xyz + x'y'z \\ &= z'(xy' + x'y) + z(xy + x'y') \\ &= z'(xy' + x'y) + z(xy' + x'y)' \\ &= z \oplus (x \oplus y) \end{aligned}$$

$$C = z(xy' + x'y) + xy = z(x \oplus y) + xy$$
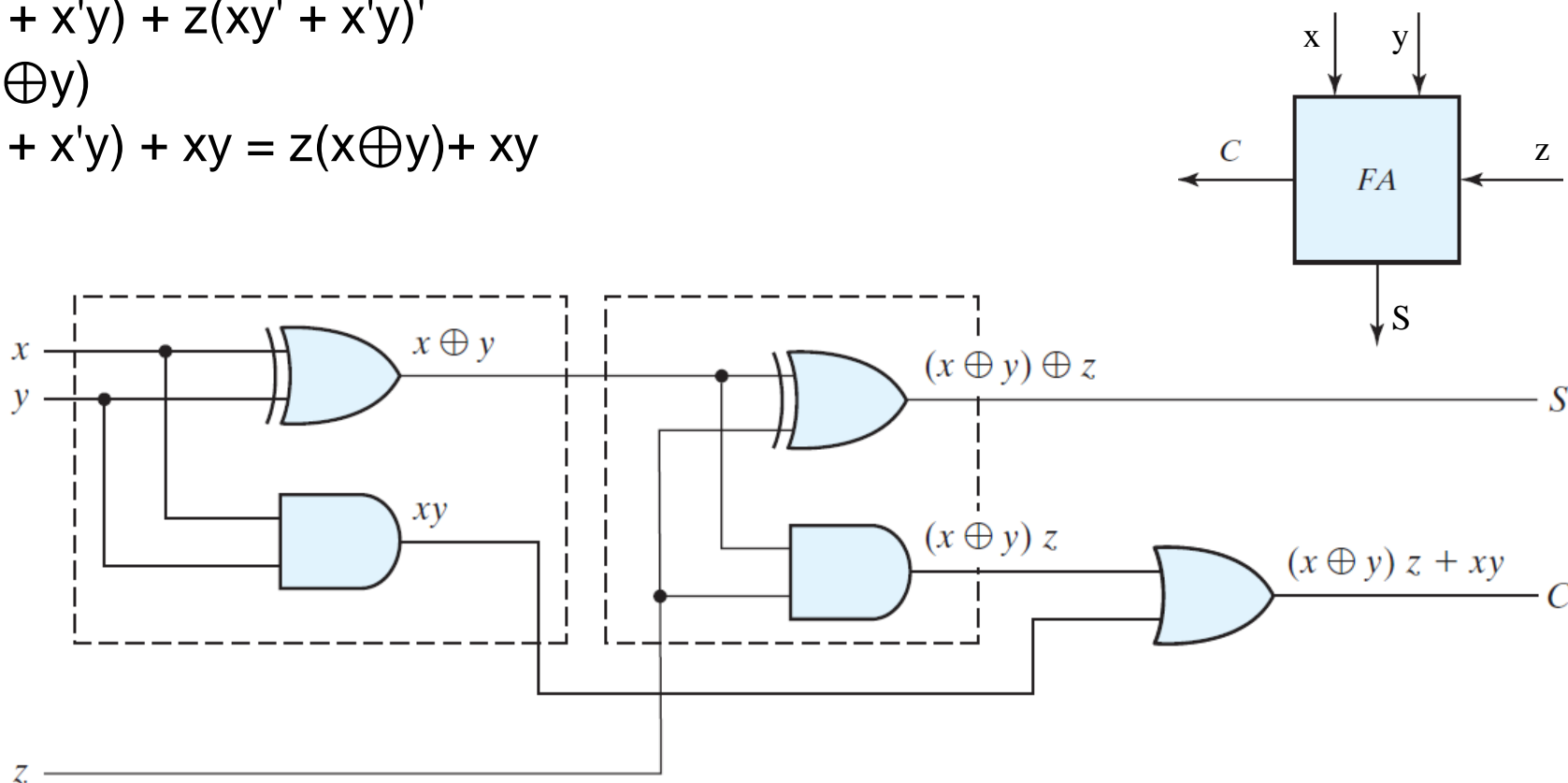
$$\begin{aligned} S &= x'y'z + x'yz' + xy'z' + xyz = x \oplus y \oplus z \\ C &= xy + xz + yz \end{aligned}$$



Ripple-Carry Adder




- unsigned addition
- $(C_n S_{n-1} S_{n-2} \dots S_0) = (A_{n-1} A_{n-2} \dots A_0) + (B_{n-1} B_{n-2} \dots B_0)$
- eg. $S = A + B$, $A = A_3 A_2 A_1 A_0$, $B = B_3 B_2 B_1 B_0$, $S = S_3 S_2 S_1 S_0$

| | | | | | |
|---|---|---|-----------|-------|---|
| | | | C_{i+1} | C_i | |
| C | 1 | 0 | 1 | 1 | 0 |
| A | | 1 | 0 | 1 | 1 |
| B | | 1 | 0 | 0 | 1 |
| S | 1 | 0 | 1 | 0 | 0 |

The computation time of a ripple-carry adder grows linearly with word length n

$T = O(n)$ due to **carry chain**

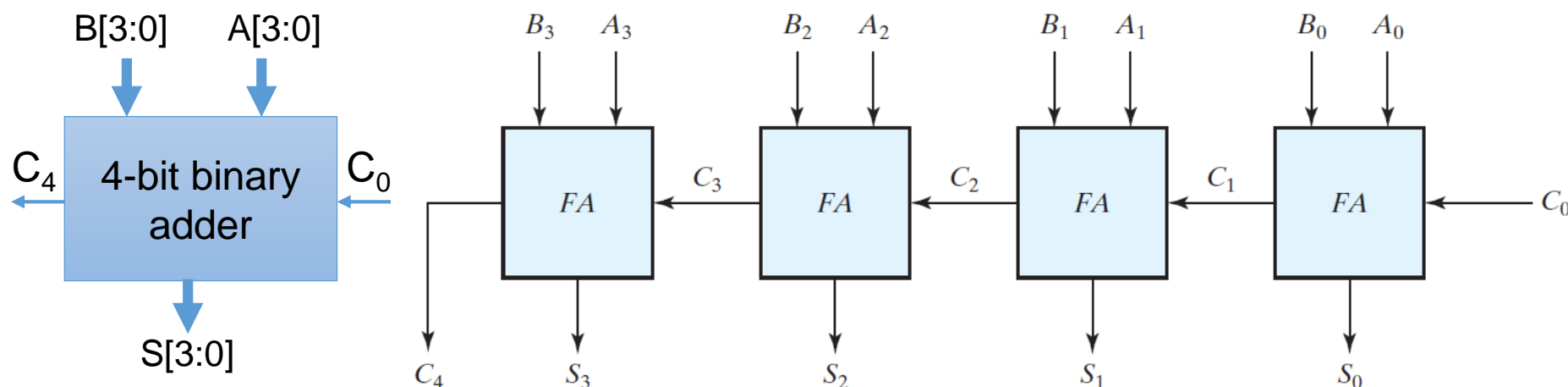

Ripple-Carry Adder


| Ai \ BiCi | | | | |
|-----------|---------|-------|---------|---------|
| | 00 | 01 | 11 | 10 |
| 0 | m_0 | 1 | m_3 | m_2 1 |
| 1 | m_4 1 | m_5 | m_7 1 | m_6 |

$$S_i = A_i \oplus B_i \oplus C_i$$

| Ai \ BiCi | | | | |
|-----------|-------|---------|---------|---------|
| | 00 | 01 | 11 | 10 |
| 0 | m_0 | m_1 | m_3 1 | m_2 |
| 1 | m_4 | m_5 1 | m_7 1 | m_6 1 |

$$C_{i+1} = A_i B_i + C_i (A_i \oplus B_i)$$

| Ai | Bi | Ci | Ci+1 | Si |
|----|----|----|------|----|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 1 | 1 |

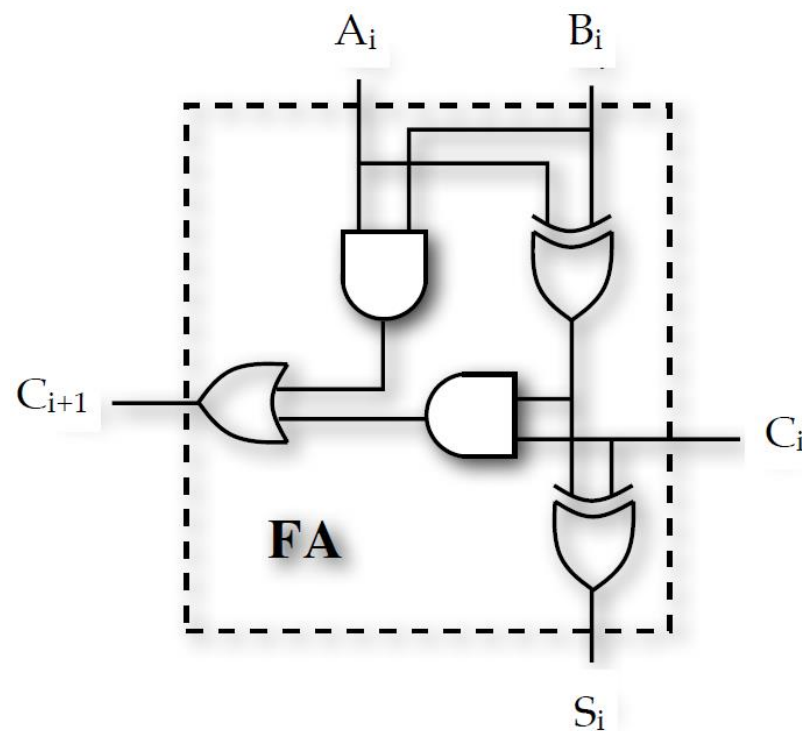

Carry Lookahead Adder

- For a full adder, define what happens to carry

- Carry-generate: $C_{out}=1$ independent of C_{in}

- $G_i = A_i \cdot B_i$

- Carry-propagate: $C_{out}=C_{in}$


- $P_i = A_i \oplus B_i$ ($P_i = A_i + B_i$)

- Use the above G_i and P_i

- $C_{i+1} = A_i B_i + B_i C_i + A_i C_i = A_i B_i + (A_i + B_i) C_i = G_i + P_i C_i$

- $S_i = A_i \oplus B_i \oplus C_i = P_i \oplus C_i$

| A_i | B_i | G_i | P_i |
|-------|-------|-------|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | x |

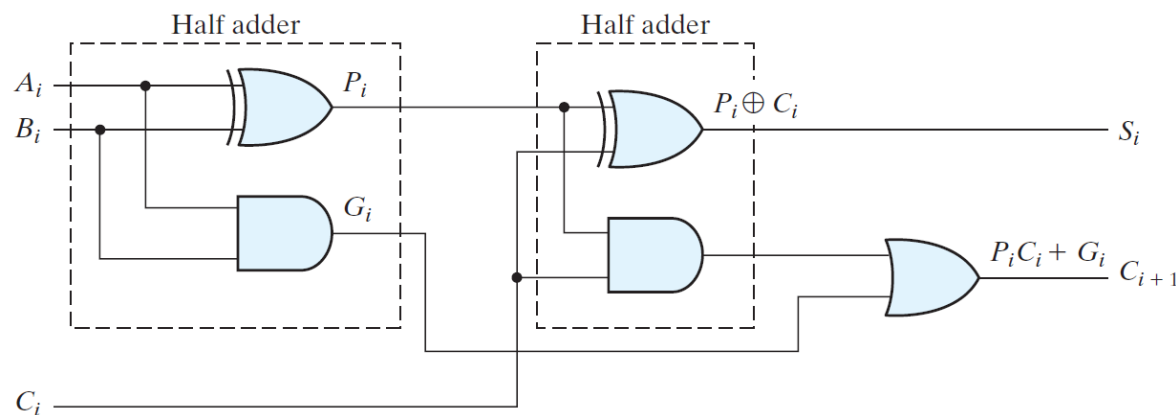

Carry Lookahead Adder

- Do not have to wait for C_i to compute C_{i+1}
 - $C_{i+1} = G_i + P_i C_i$
 - $C_{i+2} = G_{i+1} + P_{i+1} C_{i+1} = G_{i+1} + P_{i+1} G_i + P_{i+1} P_i C_i$
 - $C_{i+3} = G_{i+2} + P_{i+2} C_{i+2} = G_{i+2} + P_{i+2} G_{i+1} + P_{i+2} P_{i+1} G_i + P_{i+2} P_{i+1} P_i C_i$
 - $C_{i+4} = G_{i+3} + P_{i+3} C_{i+3} = G_{i+3} + P_{i+3} G_{i+2} + P_{i+3} P_{i+2} G_{i+1} + P_{i+3} P_{i+2} P_{i+1} G_i + P_{i+3} P_{i+2} P_{i+1} P_i C_i$
- Fixed delay time for each carry (but not the same for every gate!)
- Fanout of G_i & P_i also affect the overall delay \rightarrow usually be limited to 4 bits

C_0 =input carry,

$$C_1 = G_0 + P_0 C_0,$$

$$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0,$$

$$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$$

Carry Lookahead Adder

C_0 = input carry,



$C_1 = G_0 + P_0 C_0$,

$C_2 = G_1 + P_1 C_1 = G_1 + P_1 G_0 + P_1 P_0 C_0$,

$C_3 = G_2 + P_2 C_2 = G_2 + P_2 G_1 + P_2 P_1 G_0 + P_2 P_1 P_0 C_0$

$$G_i = A_i \cdot B_i$$
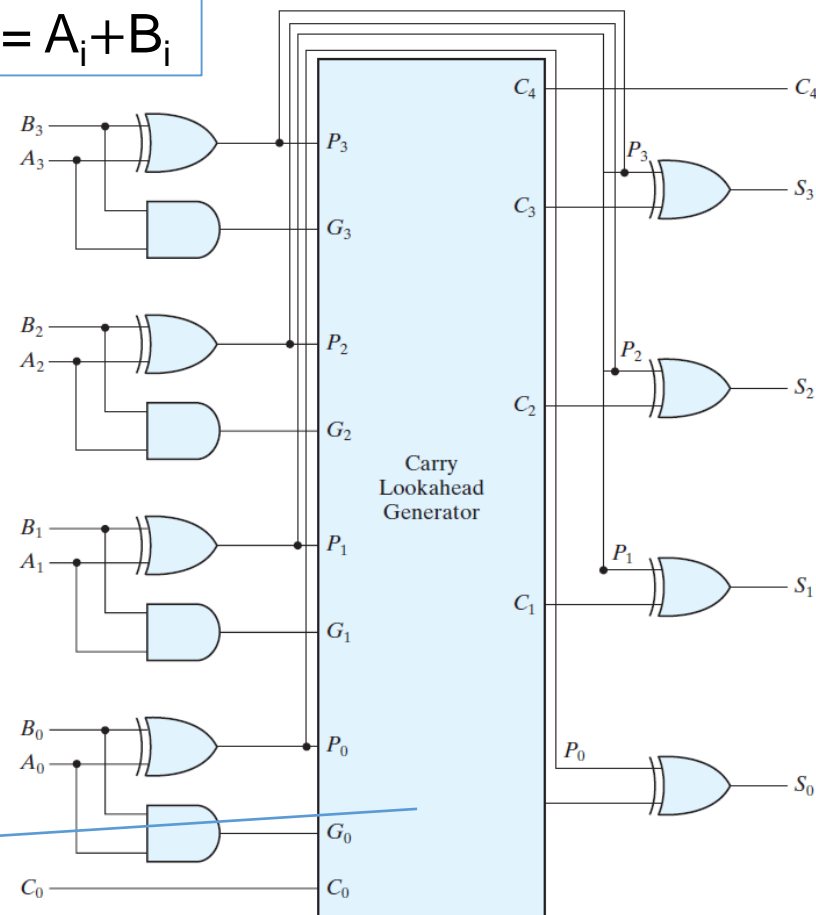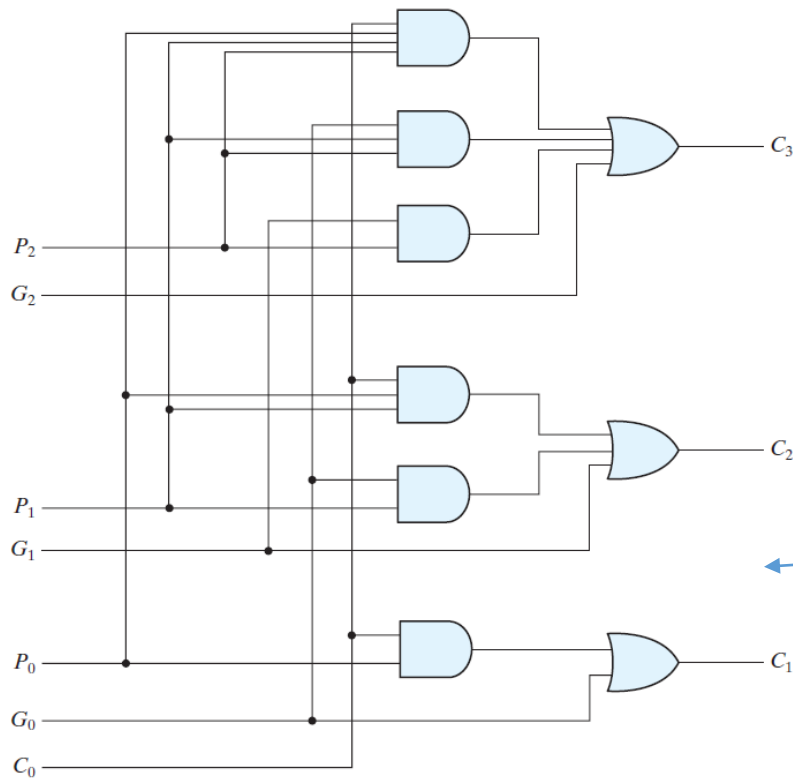
$$P_i = A_i \oplus B_i \text{ or } P_i = A_i + B_i$$




Outline

- Binary Adder
- **Binary Subtractor**
- Decimal Adder (BCD)
- Binary Multiplier
- Other Arithmetic Functions

Binary Adders/Subtractors

- Binary subtraction normally is performed by adding the minuend to the 2's complement of the subtrahend.

| M | Function | Comments |
|---|------------|-------------|
| 0 | $S=A+B$ | addition |
| 1 | $S=A+B'+1$ | subtraction |

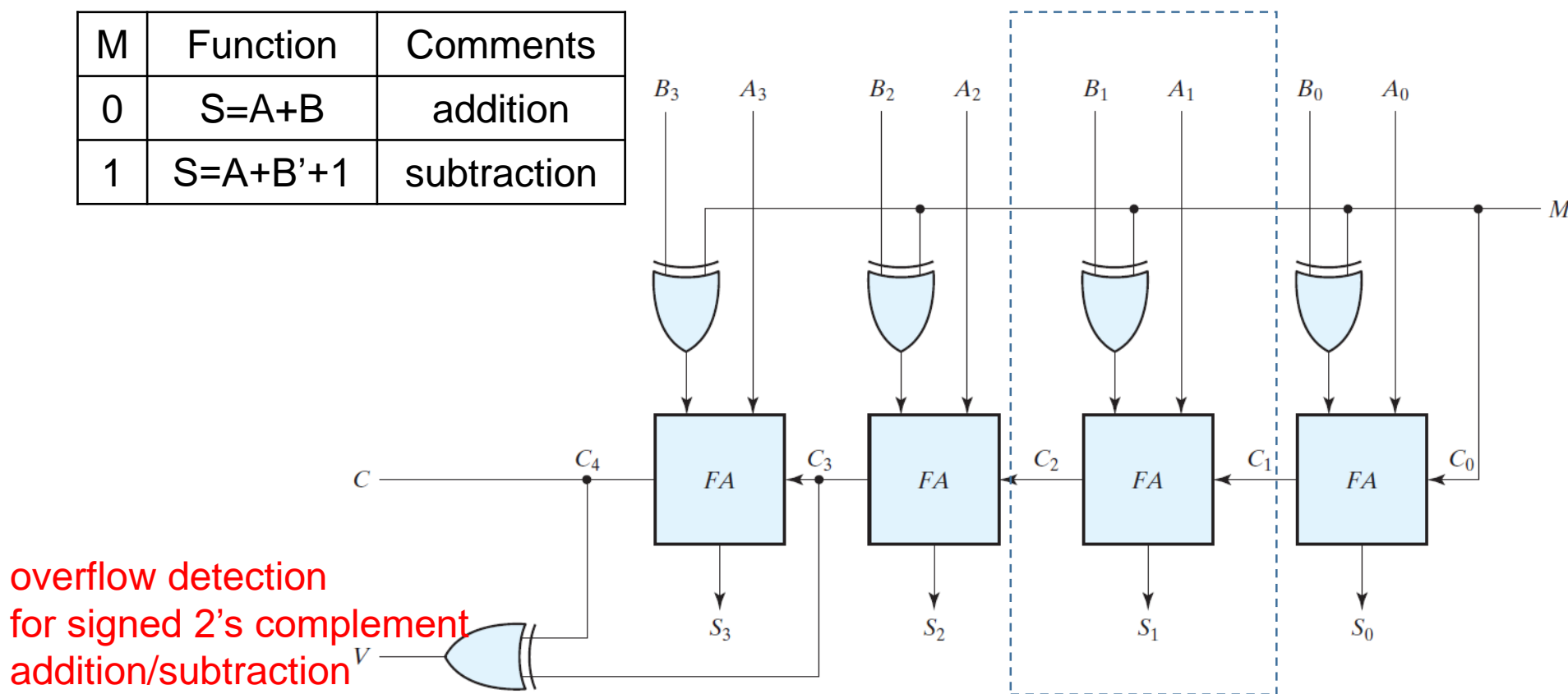

Overflow

- When n -digits addition with sum occupying $n+1$ digits, we say that an overflow (溢出) occurred.

- **Carry** for unsigned numbers:

- Carry indicates unsigned number overflow

$$\begin{array}{rcccccc}
 & 1 & 1 & 1 & & & \\
 & 1 & 0 & 1 & 1 & \dots & 11 \\
 + & 0 & 1 & 1 & 1 & \dots & 7 \\
 \hline
 1 & 0 & 0 & 1 & 0 & \dots & 18 \text{ (needs 5bits)}
 \end{array}$$

- **Overflow** for Signed numbers: (2's Complement)

- two -ve numbers are added and the obtained result is +ve
- two +ve numbers are added and the obtained result is -ve

$$\begin{array}{rcccccc}
 & 1 & 0 & 0 & 1 & & \\
 & \boxed{1} & 0 & 0 & 1 & \dots & -7 \\
 + & \boxed{1} & 1 & 0 & 1 & \dots & -3 \\
 \hline
 1 & \boxed{0} & 1 & 1 & 0 & \dots & -10 \\
 & & \underbrace{\hspace{1.5cm}} & & & & 6
 \end{array}$$


4 bits can not correctly represent -10

$$\begin{array}{cccccccc}
 & 0 & 1 & 1 & 1 & & & \\
 & \boxed{0} & 1 & 1 & 1 & \dots & 7 & \\
 + & \boxed{0} & 0 & 0 & 1 & \dots & 1 & \\
 \hline
 & \boxed{1} & 0 & 0 & 0 & \dots & 8 & \\
 & & \underbrace{\hspace{1.5cm}} & & & & & \\
 & & & -8 & & & &
 \end{array}$$

4 bits can not correctly represent +8

Binary Adders/Subtractors

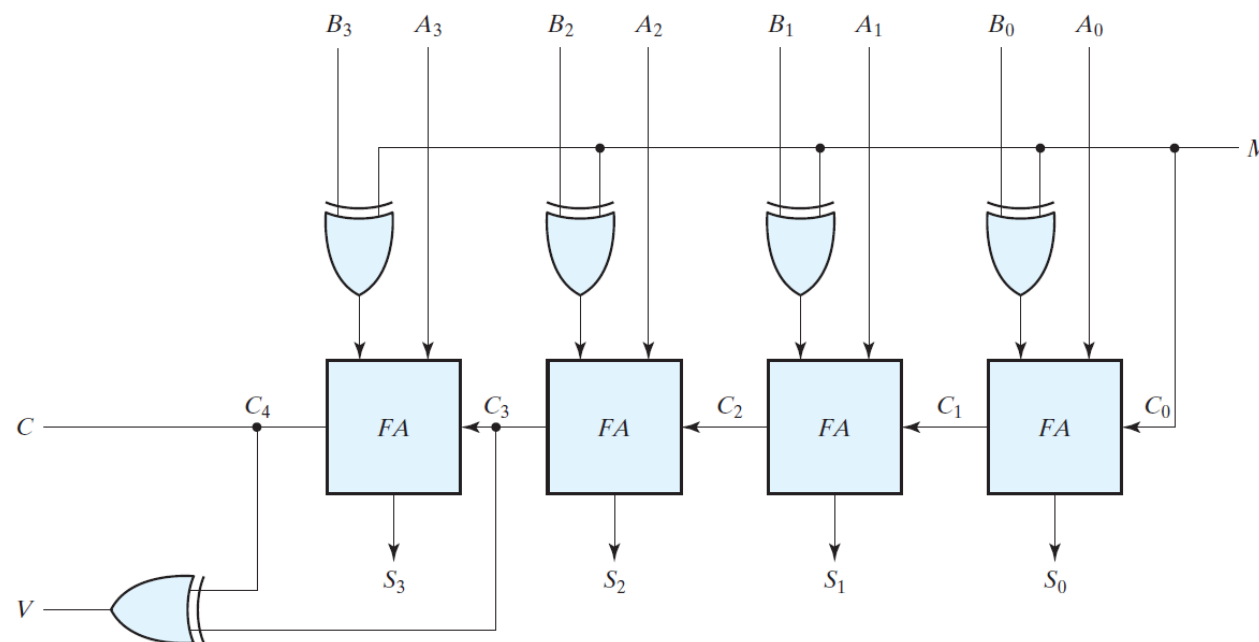
- Overflow happens when A and B are 2's complement signed value
- Example: In each case, determine the values of the four SUM outputs, the carry C , and overflow V



| M | A | B | SUM | C | V |
|---|------|------|------|---|---|
| 0 | 0111 | 0110 | 1101 | 0 | 1 |
| 1 | 1100 | 1001 | 0011 | 1 | 0 |

Serial Adder

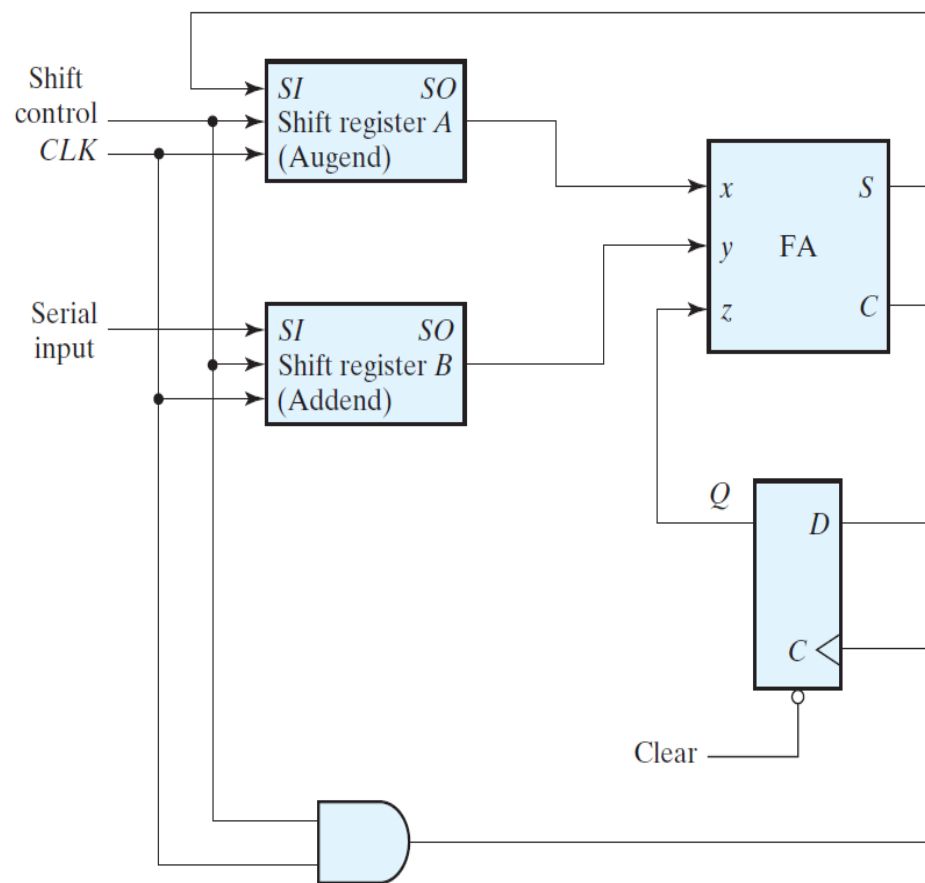
- Initially, augend is in register A and addend is in register B
- Shift control enables/disables the clock for FF
- addition of two operands from LSB to MSB
- A new sum (S) bit is transferred to shift register A
- A carry-out (C) of the FA is transferred to Q as the z input of the next addition
- Finally, when the shift control is disabled, summation result is stored in shift register A



Timing Sequence of Serial Adder

- Serial addition of 0101 + 0111
 - Register A(Store Augend and Sum): 0101
 - Register B(Store Addend): 0111
 - More cycles required to initialize Register A and B
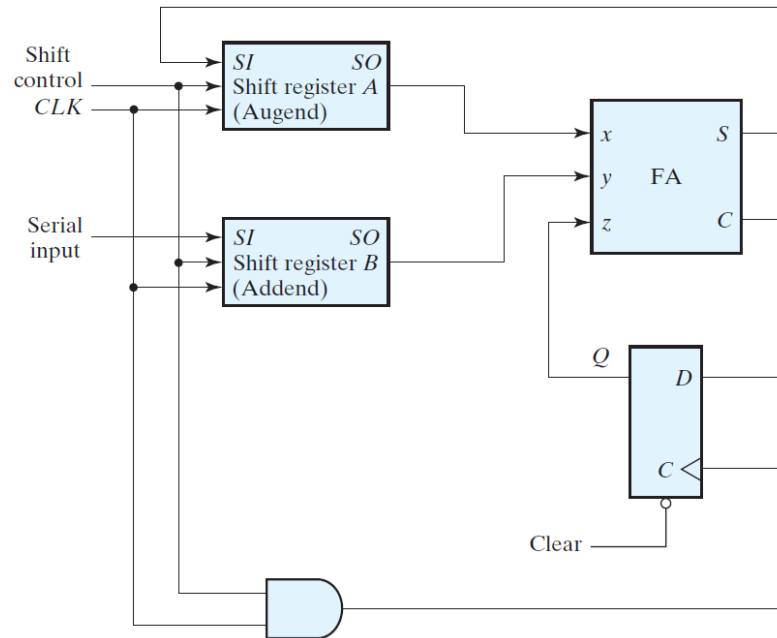
$$\begin{array}{r}
 1110 \\
 0101 \\
 + 0111 \\
 \hline
 1100
 \end{array}$$



| T | Register A(x) | Register B(y) | z(C _{in}) | S | Q(C _{out}) |
|---|---------------|---------------|---------------------|---|----------------------|
| 0 | 0101 | 0111 | 0 | 0 | 1 |
| 1 | 0010 | 0011 | 1 | 0 | 1 |
| 2 | 0001 | 0001 | 1 | 1 | 1 |
| 3 | 1000 | 0000 | 1 | 1 | 0 |
| 4 | 1100 | 0000 | 0 | 0 | 0 |

sum

Outline

- Binary Adder
- Binary Subtractor
- **Decimal Adder (BCD)**
- Binary Multiplier
- Other Arithmetic Functions

Decimal Adders

- Addition of 2 decimal digits in BCD
- $\{C_{out}, S\} = A + B + C_{in}$
- $S = S_8 S_4 S_2 S_1$, $A = A_8 A_4 A_2 A_1$, $B = B_8 B_4 B_2 B_1$
- A digit in BCD cannot exceed 9, add 6 (0110) for final correction.

| Decimal Symbol | BCD Digit |
|----------------|-----------|
| 0 | 0000 |
| 1 | 0001 |
| 2 | 0010 |
| 3 | 0011 |
| 4 | 0100 |
| 5 | 0101 |
| 6 | 0110 |
| 7 | 0111 |
| 8 | 1000 |
| 9 | 1001 |

| | | | | | | | |
|------------|----|-------|---|---|---|--------------|----------------------|
| 10 | | 1 | 0 | 0 | 0 | 0 | |
| 8_{10} | A | 1 | 0 | 0 | 0 | 0_2 | |
| 9_{10} | B | 1 | 0 | 0 | 1 | 1_2 | |
| | | <hr/> | | | | | |
| | KZ | 1 | 0 | 0 | 0 | 1_2 | binary coded results |
| | | | | | | 0 1 1 0 $_2$ | if > 9, add 6 |
| 17 $_{10}$ | CS | 0 | 0 | 0 | 1 | 0 1 1 1 $_2$ | BCD coded result |

K: binary carry, Z: binary sum, C: BCD carry, S: BCD sum

Decimal Adders

| K | Binary Sum | | | | C | BCD Sum | | | | Decimal |
|---|----------------|----------------|----------------|----------------|---|----------------|----------------|----------------|----------------|---------|
| | Z ₈ | Z ₄ | Z ₂ | Z ₁ | | S ₈ | S ₄ | S ₂ | S ₁ | |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 2 |
| 0 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 3 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 4 |
| 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 0 | 1 | 5 |
| 0 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 6 |
| 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 7 |
| 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 8 |
| 0 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 0 | 1 | 9 |
| 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 10 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 11 |
| 1 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 0 | 12 |
| 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 13 |
| 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 0 | 14 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 0 | 1 | 15 |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 16 |
| 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 17 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 18 |
| 1 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 19 |

$Z_8Z_4 + Z_8Z_2$


K

- C = 1 when
 1. K=1
 2. or K = 0, but A+B > 9, which is $Z_8Z_4 + Z_8Z_2$
- C = 1 means need to add 0110

| Z ₂ Z ₁ / Z ₈ Z ₄ | 00 | 01 | 11 | 10 |
|---------------------------------------------------------------|----|----|----|----|
| 00 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 |
| 11 | 1 | 1 | 1 | 1 |
| 10 | 0 | 0 | 1 | 1 |

Decimal Adders


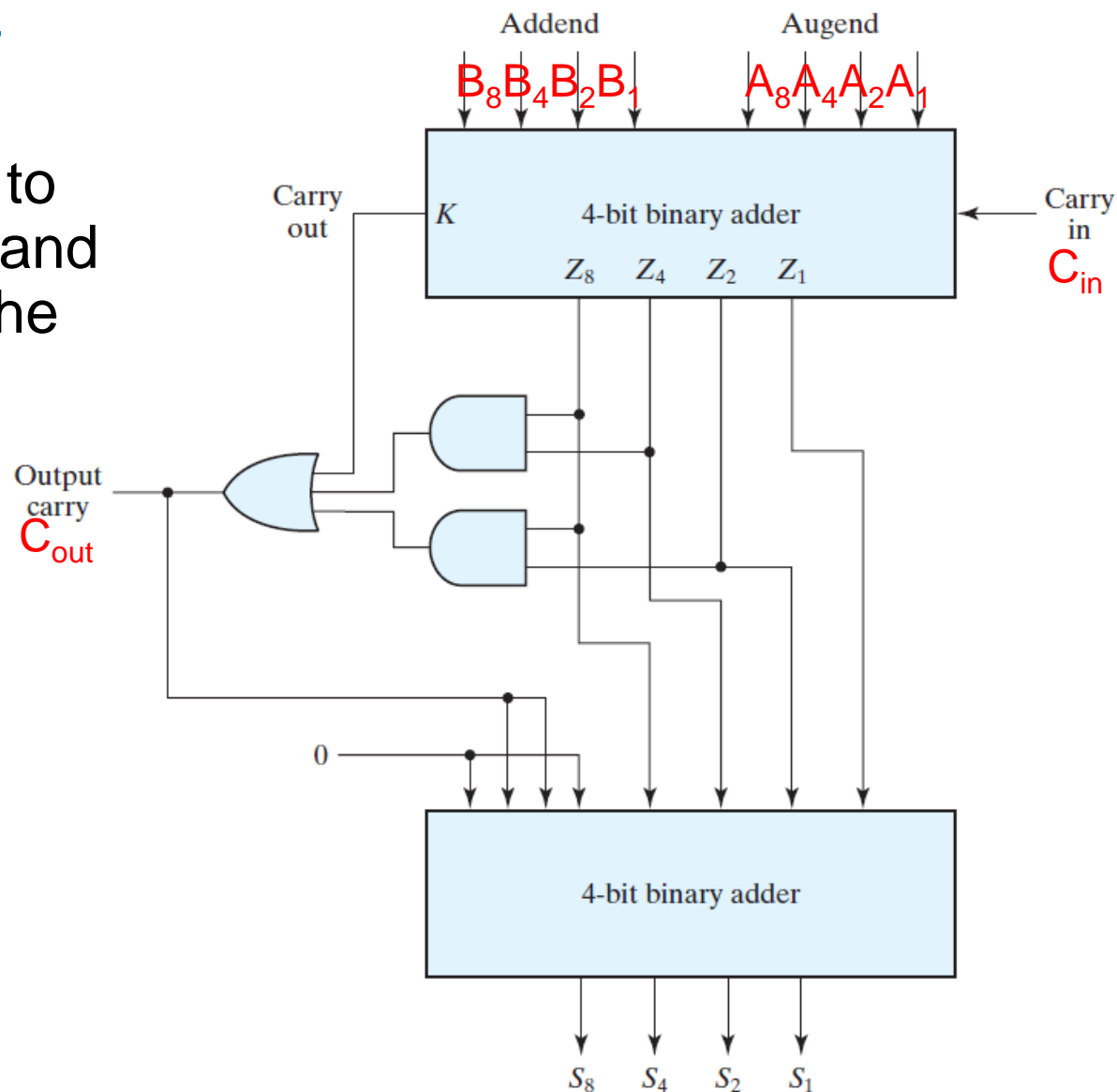
- $C_{out} = K + Z_8 Z_4 + Z_8 Z_2$
- When $C = 1$, it is necessary to add 0110 to the binary sum and provide an output carry for the next stage.




Outline

- Binary Adder
- Binary Subtractor
- Decimal Adder (BCD)
- **Binary Multiplier**
- Other Arithmetic Functions

2-bit x 2-bit Binary Multiplier

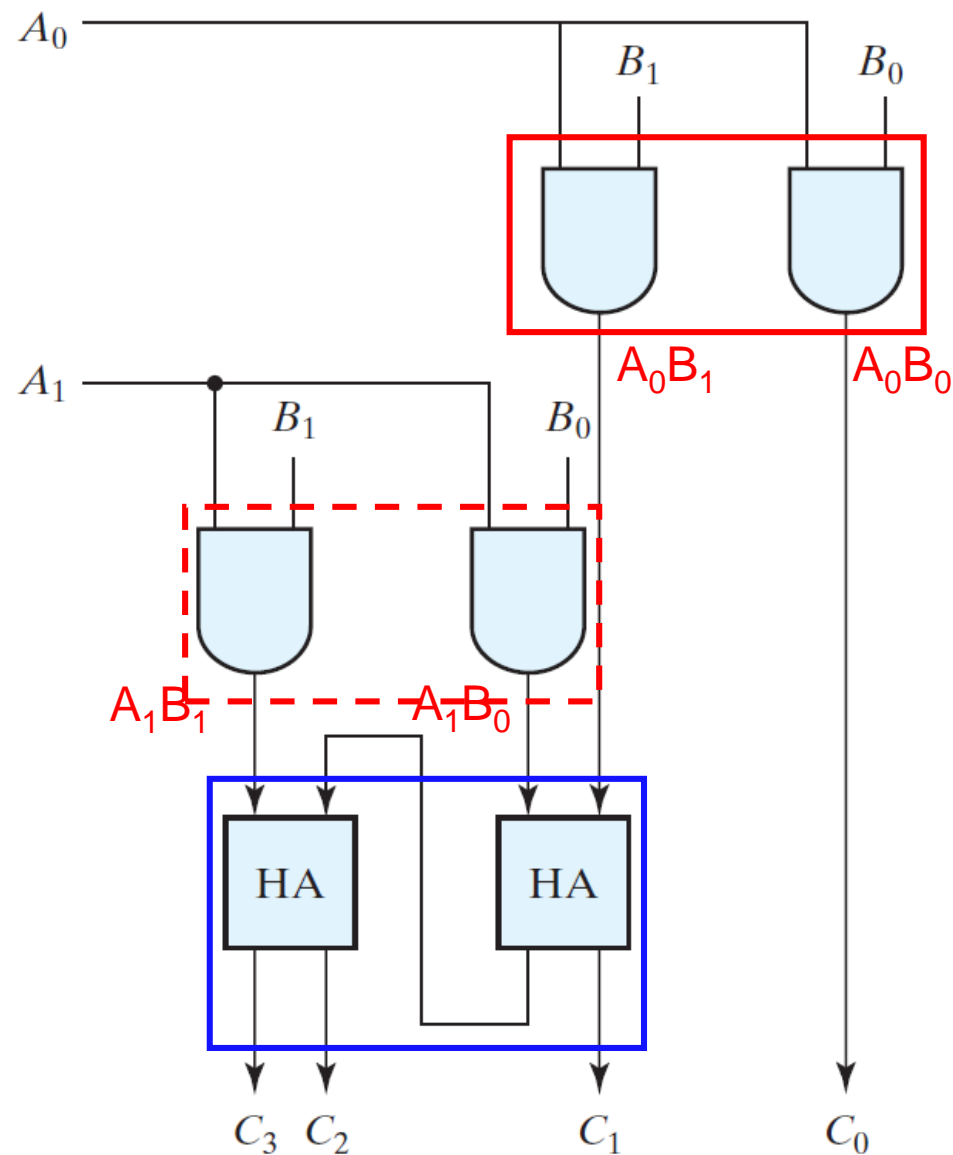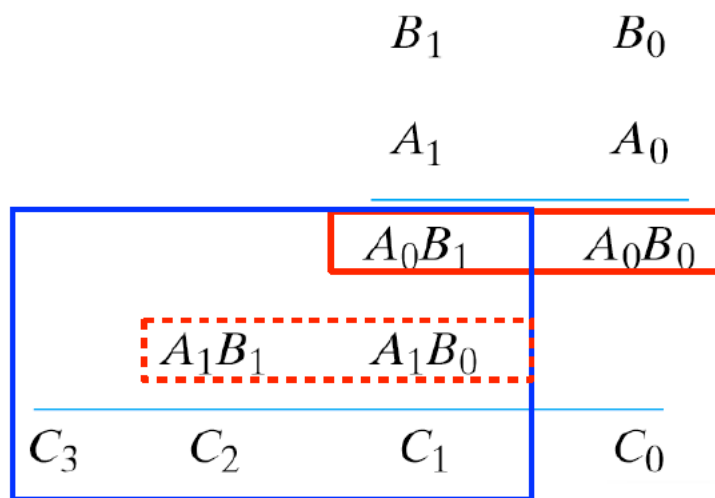

4-bit x 3-bit Binary Multiplier

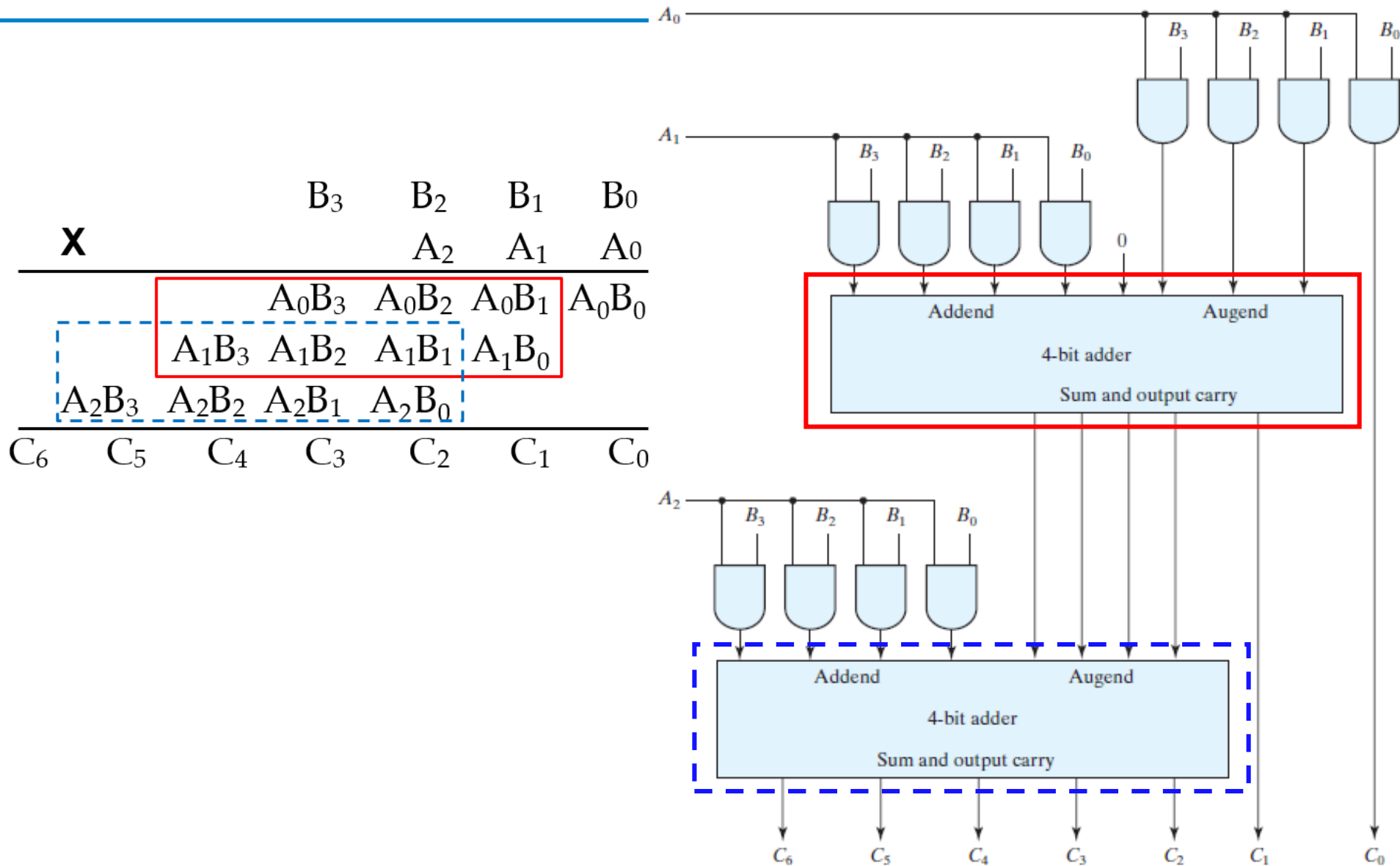

Outline

- Binary Adder
- Binary Subtractor
- Decimal Adder (BCD)
- Binary Multiplier
- **Other Arithmetic Functions (optional)**

Other Arithmetic Functions


- It is convenient to design the functional blocks by **contraction**
 - Removal of redundancy from circuit to which input fixing has been applied
- Functions
 - Increment
 - Decrement
 - Multiplication by constant
 - Division by constant
 - Zero fill and extension

Design by Contraction


- Simplify the logic in a functional block to implement a different function
 - The new function must be realizable from the original function by applying basic functions to its inputs
 - Contraction is treated here only for application of 0s and 1s (not for X and X')
 - After application of 0s and 1s, equations or the logic diagram are simplified

Design by Contraction Example

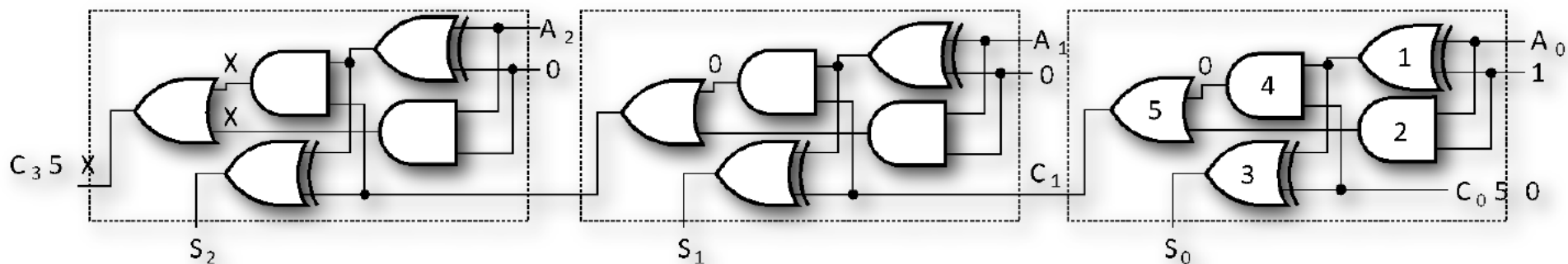- Contraction of a ripple carry adder to incrementer for $n=1$ ($A_2A_1A_0+001$)



(a)

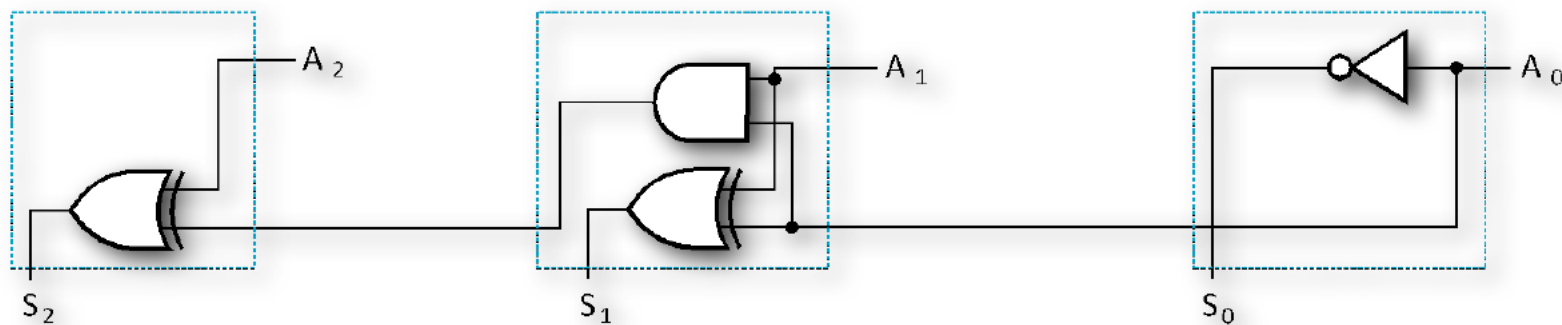


Incrementing and Decrementing


- Incrementing
 - Add a fixed value to an arithmetic variable
 - Fixed value is often 1, called counting up
 - $A+1$, $B+4$
 - Functional block is called incrementer
- Decrementing
 - Subtracting a fixed value from an arithmetic variable
 - Fixed value is often 1, called counting down
 - $A-1$, $B-4$
 - Functional block is called decrementer

Multiplication/Division by 2^n

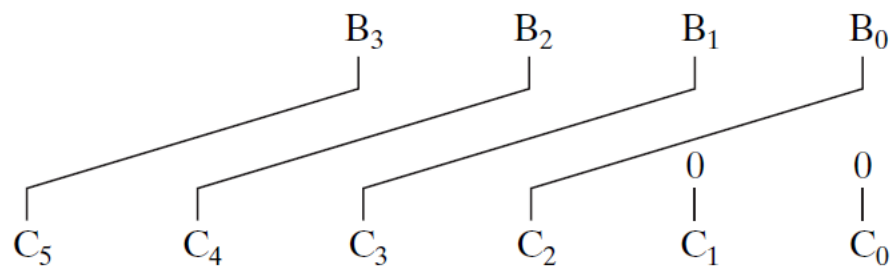- Shift left (multiplication) or right (division)




shift left by 2

 

shift right by 2

Multiplication by a Constant

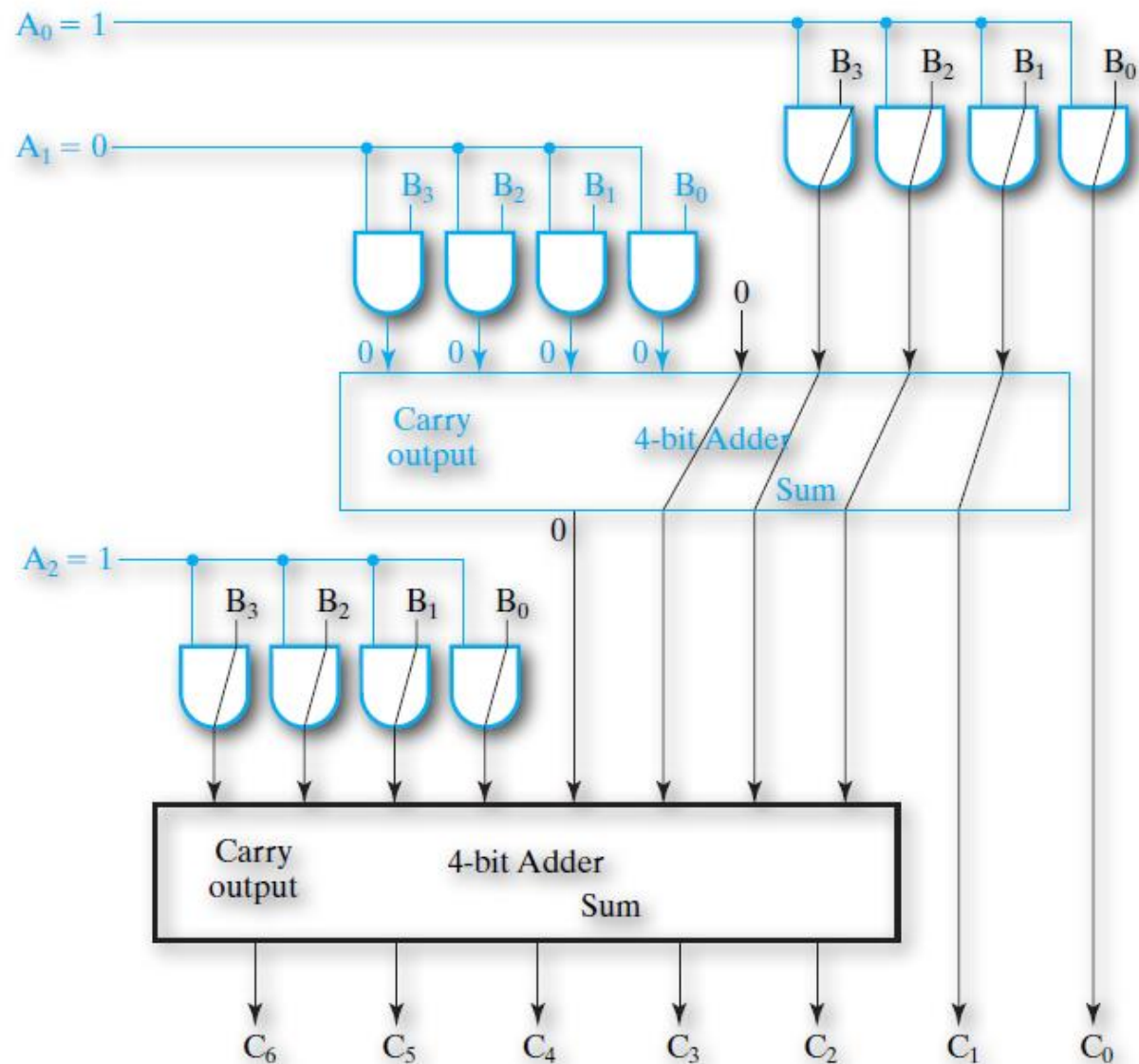- 4-bit x 3-bit Binary Multiplier
- $B_3B_2B_1B_0 \times 101$



Zero/Sign Extension

- Fill an m-bit operand with 0s to become an n-bit operand with $n > m$
 - Filling usually is applied to the MSB end of the operand
- Zero Extension
 - 01110101 filled to 16 bits
 - 0000000001110101 $\{\{8\{0\}\}01110101\}$
 - 11110101 filled to 16 bits
 - 0000000011110101 $\{\{8\{0\}\}11110101\}$
- Sign Extension
 - Copies the MSB of the operand into the new positions
 - 01110101 extended to 16 bits
 - 0000000001110101 $\{\{8\{a7\}\}a71110101\}$
 - 11110101 extended to 16 bits
 - 1111111111110101 $\{\{8\{a7\}\}a71110101\}$